

Noisemaker Workshop

Ring Modulation and Oscillator Sync (and more!)

May 14, 2009

Outline

Ring Modulation

Sync and Pulse-width Modulation

Outline

Ring Modulation

Sync and Pulse-width Modulation

Real Ring Modulation

What is it?


- ▶ Combine two signals into one by multiplying their voltages
- ▶ Ring modulation creates a signal with the sum and the difference of the input signals
- ▶ Stripped-down example: Two sine waves, 100 Hz and 600 Hz
- ▶ Ring-modulating them results in a two tones superimposed: one at 500Hz (the difference) and one at 700 Hz (the sum)
- ▶ Neat property: if you ring-modulate a signal with another (carrier) then ring-modulate the result with the carrier again, you get the original signal back
- ▶ Cool use: carrier is a noisy stream, can use to encode audio
- ▶ Pedestrian use: radio transmitters ring-modulate the audio signal with a RF carrier, receivers ring-modulate with the carrier to get audio back (tuning)

XOR "Ring Modulation"

XOR Logic

- ▶ The XOR ("exclusive or") function gives an output that's high when one or the other oscillator is high, *but not both*
- ▶ Logic Table:
0 0 → 0
1 0 → 1
0 1 → 1
1 1 → 0
- ▶ XOR'ing makes new frequencies like true ring modulation. Sometimes they're harmonically related, sometimes not.
- ▶ XOR'ing also has the encode/decode property of real ring modulation, but for digital signals

XOR Ring Modulation Circuit

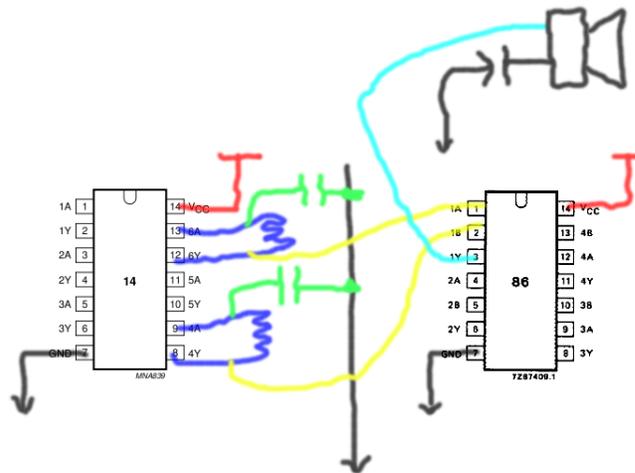

Outline

Ring Modulation

Sync and Pulse-width Modulation

Sync

Saw this before?


- ▶ Use a diode (valve) to reset one oscillator from the output of another
- ▶ Fun noises when you change the sync'ing frequency
- ▶ I mention this again, because it's fun with ring modulation

Pulse-Width

Creating non-symmetric oscillations

- ▶ To create a pulse, connect output of one oscillator to the input of the other with a capacitor
- ▶ The capacitor passes a small bit of current at the start of the pulse, but none of the low-frequency stuff
- ▶ Then use a resistor to keep the input high most of the time
- ▶ How quickly the input goes high again (after a low pulse through the cap) depends on the value of a resistor that pulls it high
- ▶ Pulse-width modulation by changing resistor makes phaser sounds

Sync

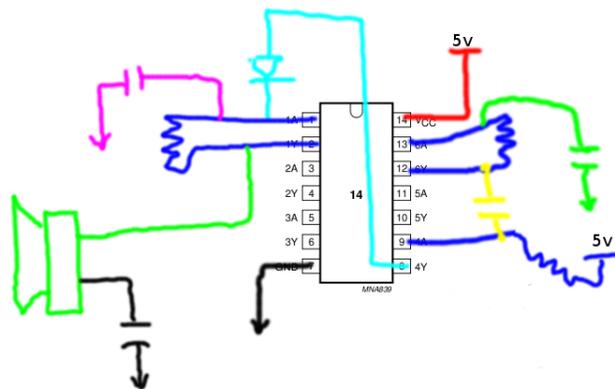

Sync with Multiple Oscillators

More fun

- ▶ If you're syncing a bunch of oscillators, makes a neat sound
- ▶ Plus, it's sweet to ring-modulate the results
- ▶ Make the sync pulse very thin, nearly instant
- ▶ Take the pulse out (cyan line in the above circuit), link it in to other oscillators with a bunch of diodes.

Diode Mixing

As long as we're talking about diodes...

- ▶ Run output of two oscillators together into same output, it's just like playing them through two speakers
- ▶ Instead, combine them with two diodes, and they add together but never subtract.

The End

[← Outline](#)