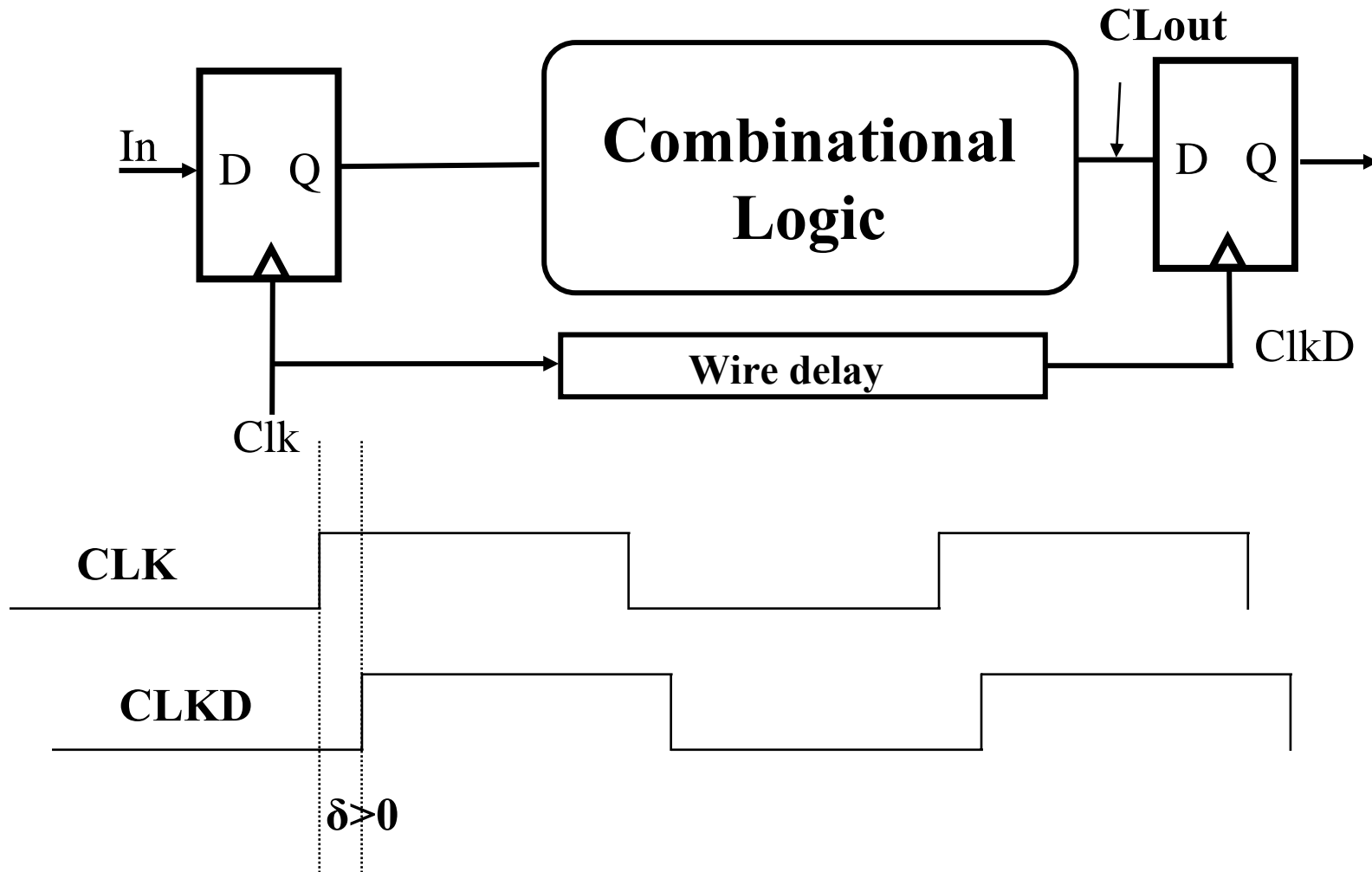


review


$$v_{out}(t) = (1 - e^{-t/\tau}) V$$

$$t_p = \ln(2) \tau = 0.69 RC$$




$$T > T_{cq} + T_{logic} + T_{su} - \delta$$
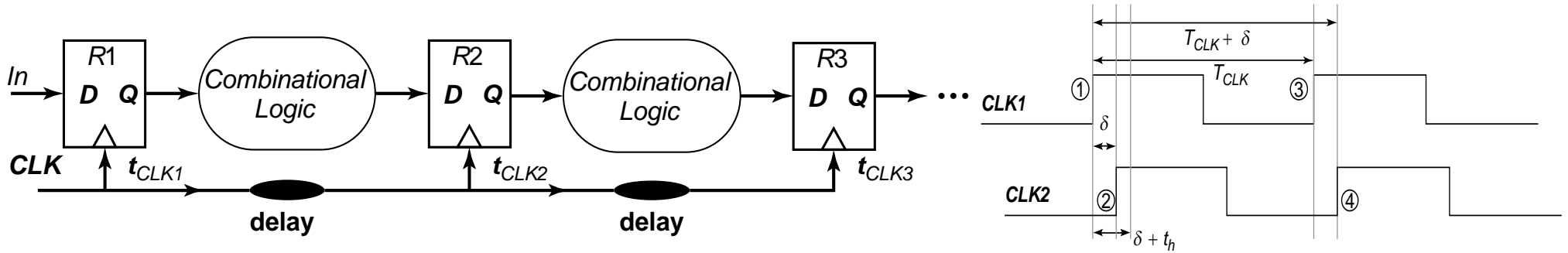
$$T_{cq,cd} + T_{logic,cd} > T_{hold} + \delta$$



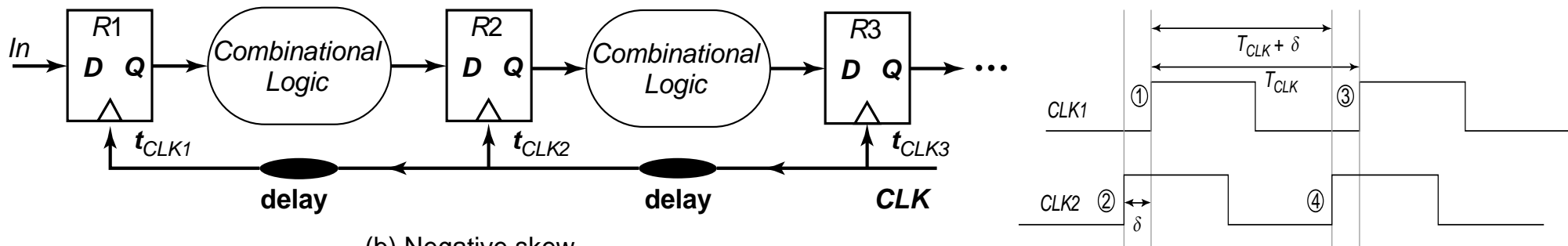
(a) Positive skew

Launching edge arrives before the receiving edge



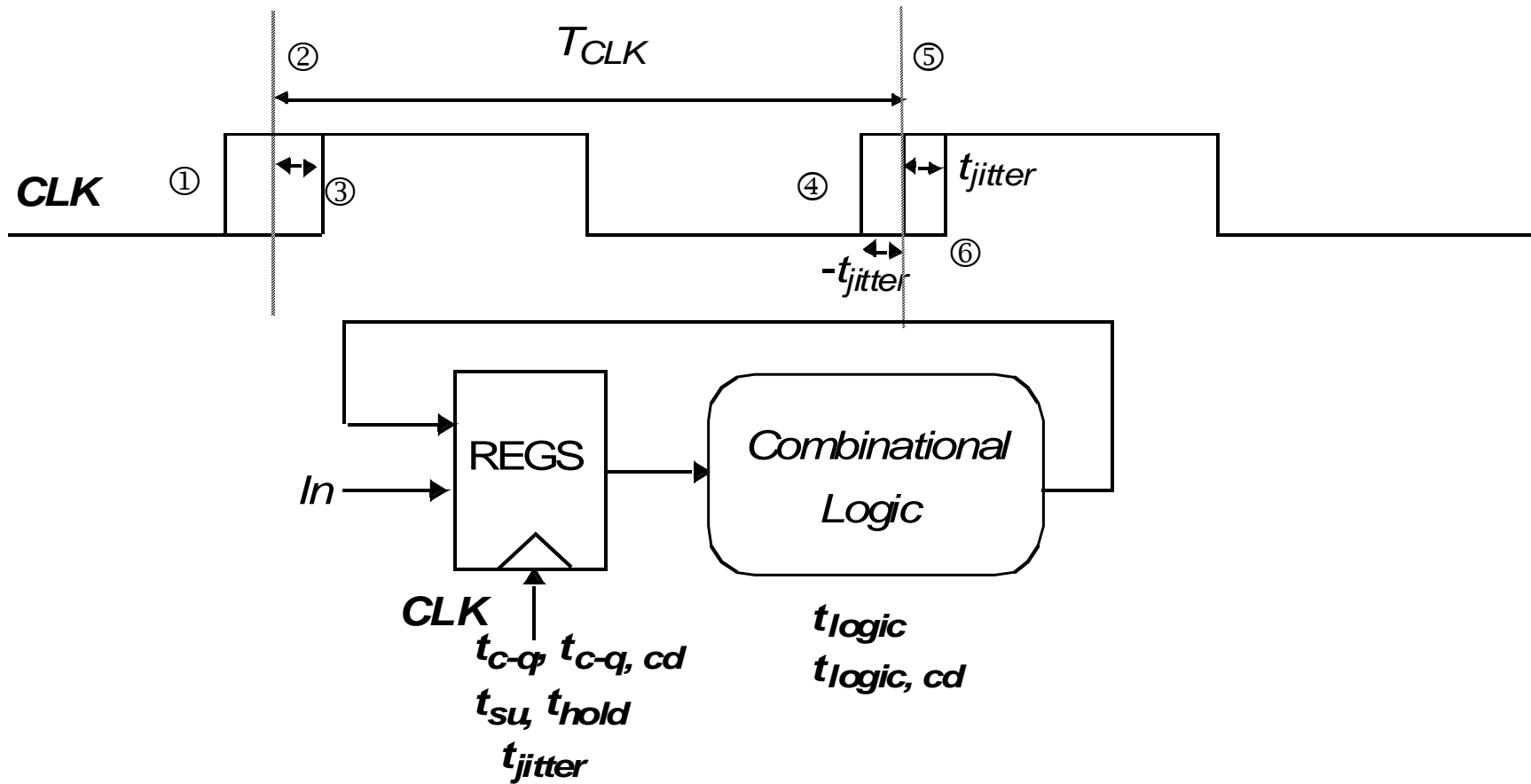(b) Negative skew

Receiving edge arrives before the launching edge



$$T_{CLK} - 2t_{jitter} > t_{c-q} + t_{logic} + t_{su}$$

or

$$T > t_{c-q} + t_{logic} + t_{su} + 2t_{jitter}$$